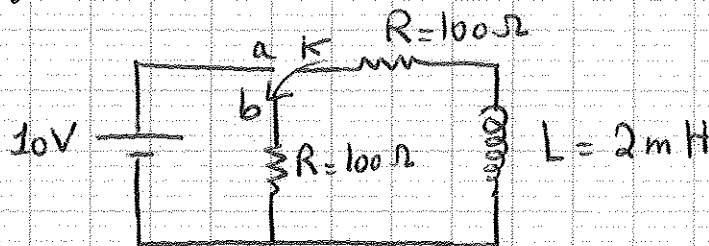


## Electromagnetism and Waves II (phys 380)

### Quiz IV.

I) The switch in figure below has been in position a for a long time. It is changed to position b at  $t = 0$ .

- (a) What is the current in the circuit at  $t = 5 \mu\text{s}$ .  
 (b) At what time has the current decayed to 1% of its initial value?



II) A metal rod is forced to move with constant velocity along two parallel metal rails. A magnetic field  $B = 0.35 \text{ T}$  points out of page.

- (a) Given:  $L = 25 \text{ cm}$ ,  $v = 0.55 \text{ m/s}$ .  
 What emf is generated?  
 (b) If rod has resistance  $R = 18 \Omega$ , what is the current in the rod?  
 (c) At what rate is energy being transferred to thermal energy?

